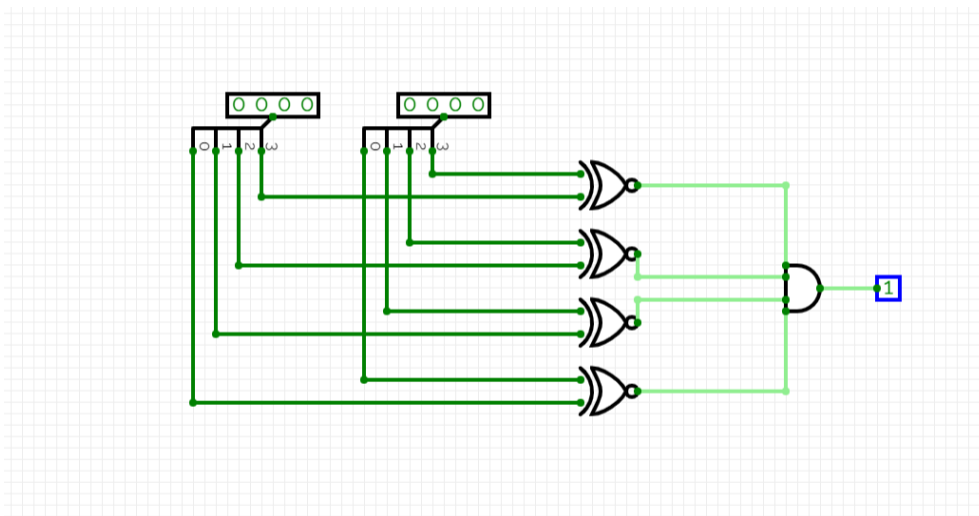


STATE DIAGRAM

It did not mention Reset in the question, but I added it. Because the system needs to be reset.



The sub-circuit which I use in my circuit. It makes a comparison and outputs 1 if it is equal.

